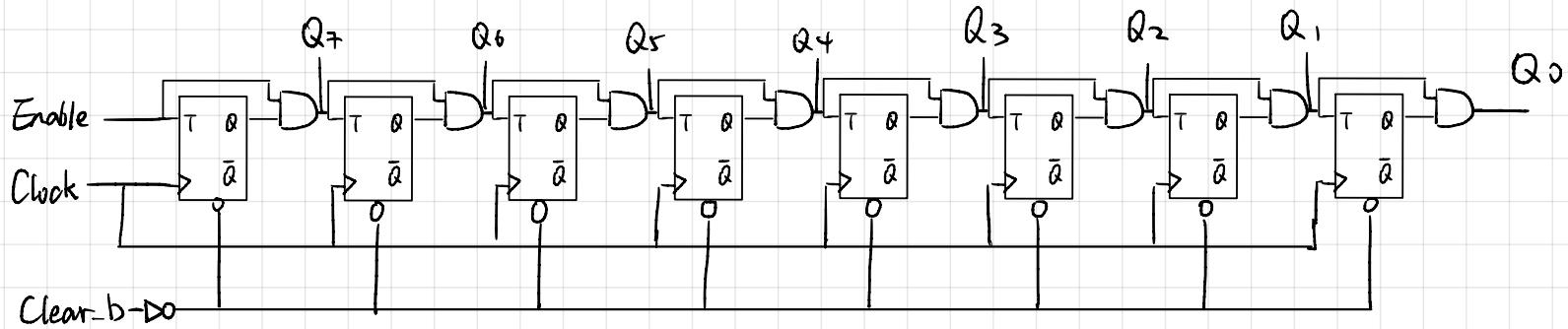


# CSC 258 LABS


lichen 65 1004767558

## Part 1


1.2.




5. Clock 1 time

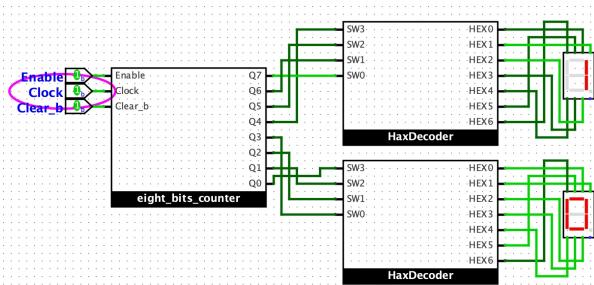


2 times

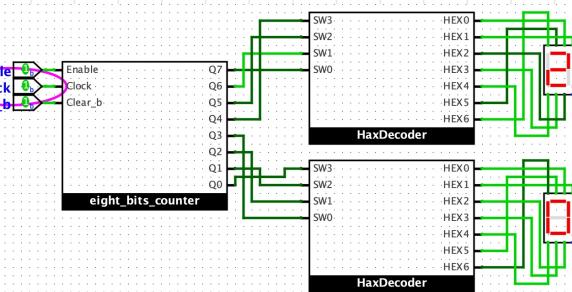


3 times

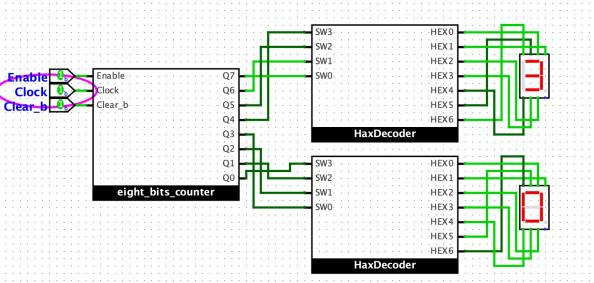


4:

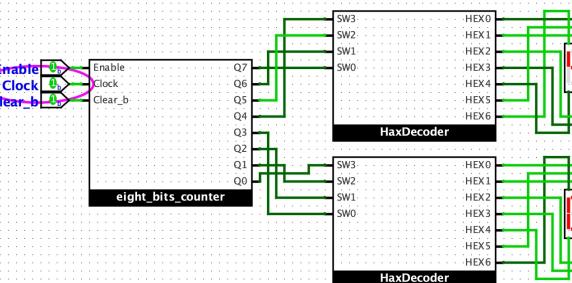


5:

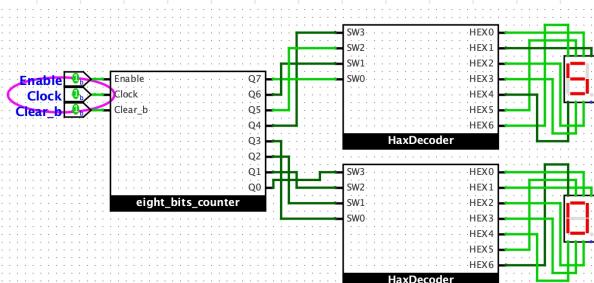

6:

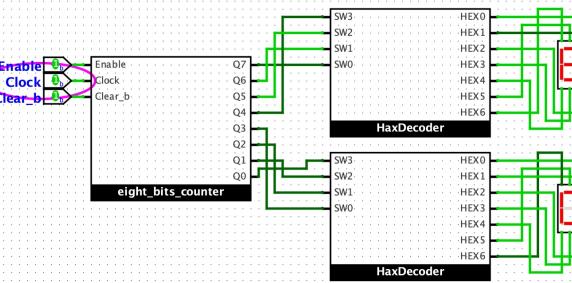


## Part 2

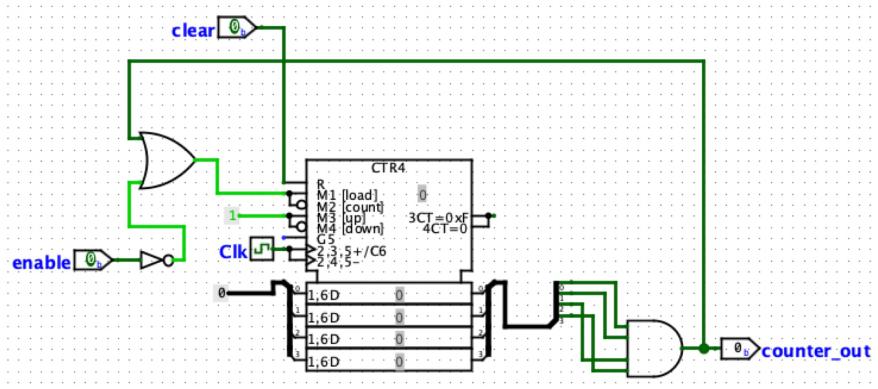

1. The check for the maximum value is not necessary in the example above. Explain why in your prelab report (**PRELAB**)
2. If you wanted this 4-bit counter to count from 0-9, how would you adjust the circuit above? (**PRELAB**)
3. In *Properties* there is a setting called *Action On Overflow*. Explain how each value for this setting responds to overflow by experimenting with this setting and describing the results. (**PRELAB**)

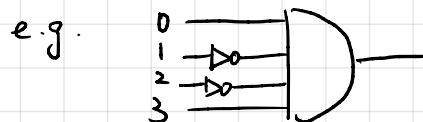1. For educational purpose , the max value part explicitly shows how reloads work when reaches the max value .
2. We can change the right part from detect 1111 to 1001 :



Then the circuit will reload when counter count to 9 .

3. Wrap Around:

the next value is 0 if incrementing  
and max value if decrementing

Stay at value: remains at max / 0



Continue counting: continue incrementing / de

load next value : the next value is loaded from input .

In your prelab report, calculate how large a counter would be required to count 50 million clock cycles, as illustrated by Figure 3. How many binary bits would that counter need to represent such a value? (**PRELAB**)

$$\lceil \log_2 50,000,000 \rceil = 26$$

# 1. Draw Schematic

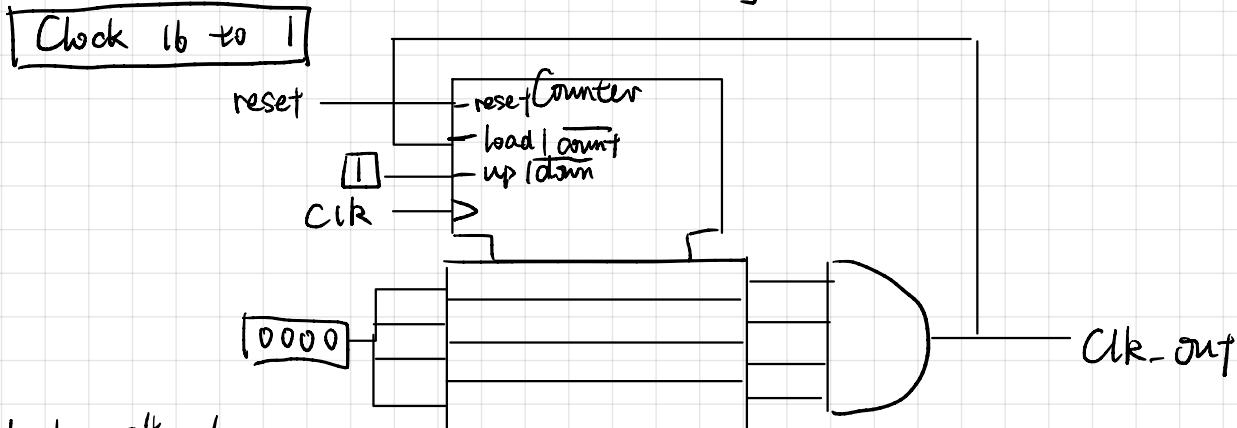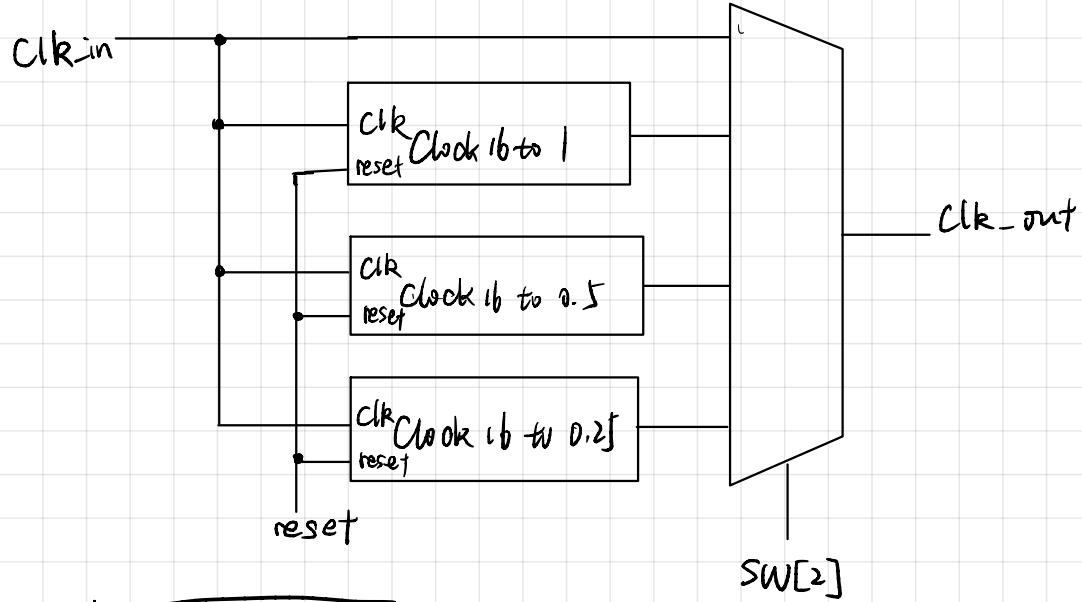

$$4 \text{ databits } 2^4 = 16$$

$$3 \text{ databits } 2^3 = 8$$

$$5 \text{ databits } 2^5 = 32 \rightarrow 16/32 = 0.5 \text{ Hz}$$

(16 Hz = 16 ticks per second) (16 cycles per second)

Duration of  
 $\text{Clk}_{\text{out}}$



Duration of  
 $\text{Clk}_{\text{out}}$ .

## 3. Test Cases :

When $\text{SW} = 00$	16 Hz
$\text{SW} = 01$	1 Hz
$\text{SW} = 10$	0.5 Hz
$\text{SW} = 11$	0.25 Hz

1/16	1/16
2	1
4	2
8	4

After F is 0 :

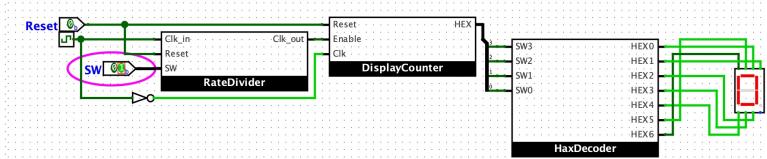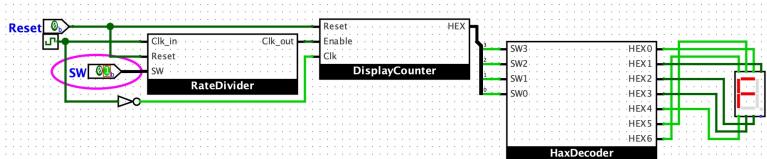


## Part 3

### LUT

Hex:


Letter	Morse Code	Pattern Representation (sequence length is 13 bits)	Hex:
000	S	• • •    3+2=5	1500
001	T	—    3	1C00
010	U	• • —    5+2=7	15C0
011	V	• • • —    6+3=9	1570
100	W	• — —    7+2=9	1770
101	X	— • • —    8+3=11	1D5C
110	Y	— 3 • 1 3 3    (13)	1D77
111	Z	— — • •    (11)	1DD4

2. Draw the schematic

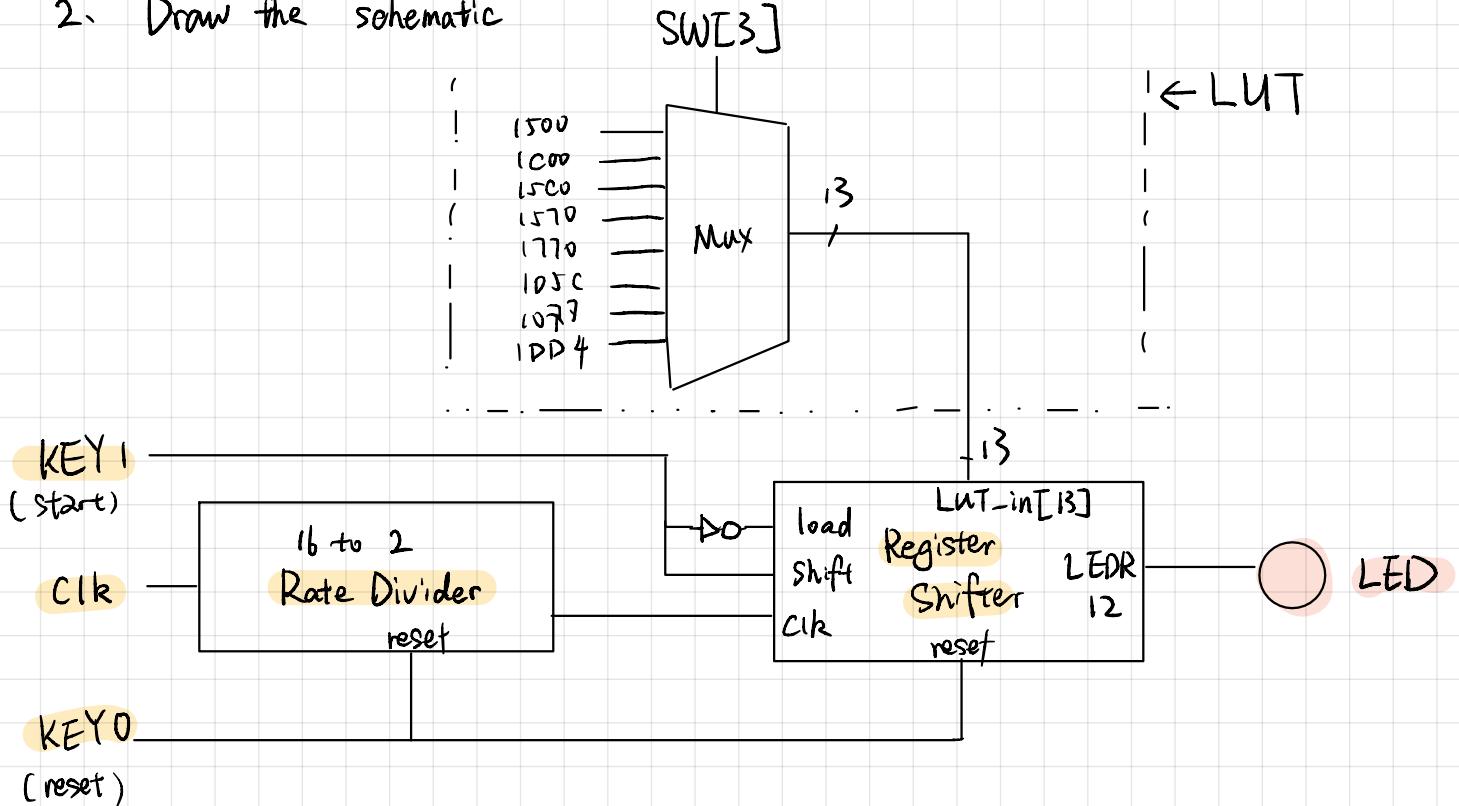


4. Test

Vector

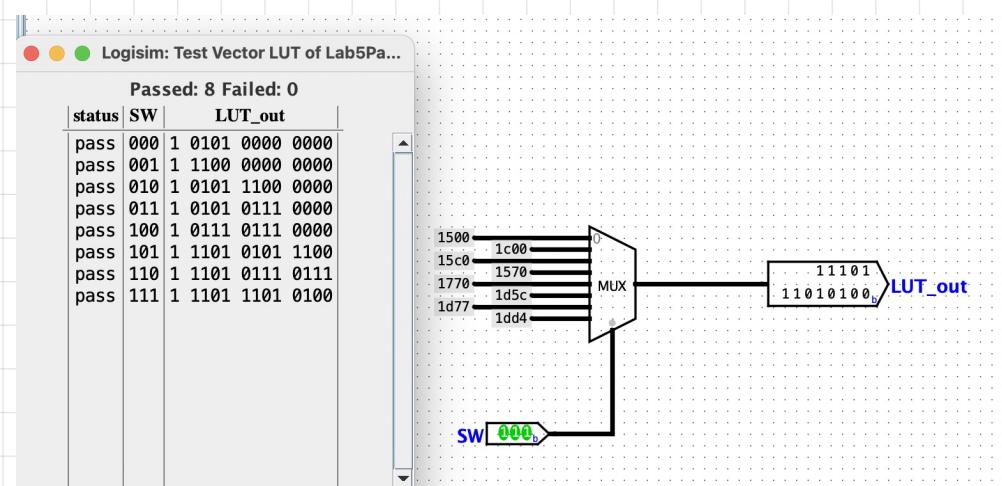


## Test cases :

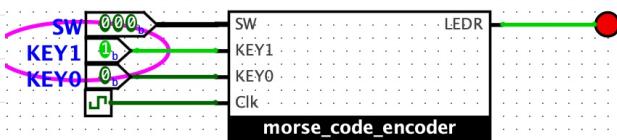


000 :

three shorts

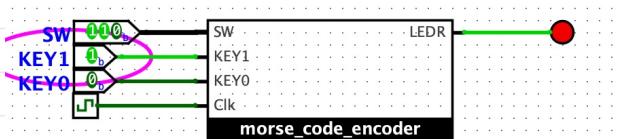

110 :

long short long long

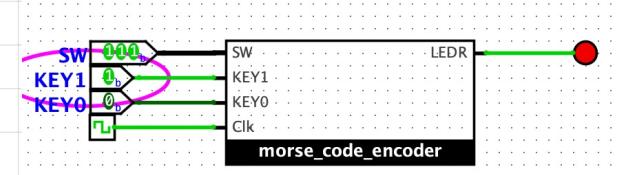

111 :

long long short short