



# Lab 3 Preparation

# What this lab requires


- More practice with Logisim, and explore some new components.
  - Arithmetic operators!
- Implementing some logical devices.
  - Full adder circuit, ALU.
- Learning some hierarchical design.
  - Mux + adders = ALU.

# Part 1: Mux + Splitter

- In components, you can find mux under the category **Plexer**. Just drag and drop on your canvas.
- Key points:
  - In Properties of the multiplexer:
    - Adjust the number of select bits to change the size of the multiplexer.
    - Adjust the number of data bits to match the size of the input data.
 
# Part 1: Mux + Splitter


- What you're supposed to do:
  - ▣ Multi-bit input into 7-to-1 mux.



## Part 2: Ripple Carry Adders


- Implement a Ripple Carry Adder by connecting (chaining) four full-adders together.
  - Must use hierarchical design!

$b$	$a$	$c_i$	$c_o$	$s$
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

 

 
# Part 3: ALU

- The ALU (**Arithmetic Logic Unit**) uses a mux to choose a single output value from a series of modules.
  - Each of these multiplexer inputs is connected to a module that performs a single arithmetic or logical operation.
- Once each operation module has been implemented with general inputs  $A$  and  $B$ , connect these ALU inputs to the switches and the ALU outputs to both the LEDs and 7-segment display (in hexadecimal).
  - Try to you reuse the modules you made in Lab 2.
  - The handout includes syntax for some new (and potentially useful) operators


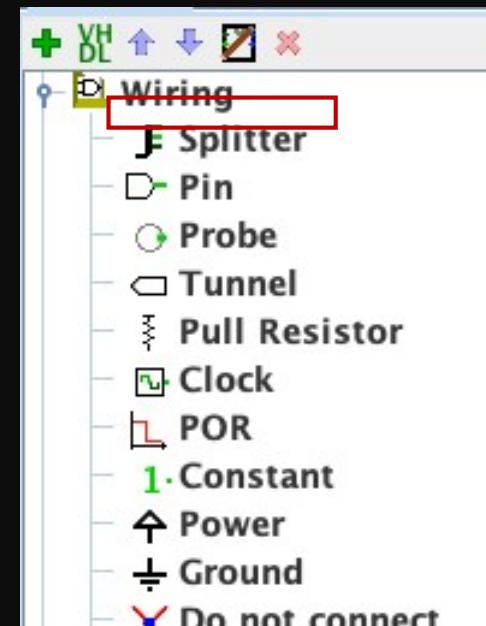
# Splitter in Logisim

- Splitter can be very useful in Logisim. You can find them under Wiring in components.
- They can be used in two ways:
  - Separating a multi-bit signal,
  - Concatenating signals together.



# Bitwise Operations

## ■ Bitwise Operations

- If you use a bitwise operation with two n-bit operands, the result is also an n-bit vector.
- For example:

0101 & 0011 → 0001

- More general mathematical notation:
  - $(X_{n-1}X_{n-2} \dots X_1X_0 \text{ \& } Y_{n-1}Y_{n-2} \dots Y_1Y_0)$  results in  $W_{n-1}W_{n-2} \dots W_1W_0$  where  $W_i$  is  $(X_i \text{ \& } Y_i)$  for every  $i$  in  $[0, n-1]$ .
- ## ■ In Logisim, this can be achieved using Splitter.
- For a bitwise AND:
    - Split the signal into separate bits,
    - Use AND gates on each pair of bits,
    - Concatenate the result bits together



# Reduction Operators

- **Reduction Operations** have the same approach as bitwise operations, but
  - They take **a single** multi-bit operand, and
  - The result is a **single-bit output**.
- In Logisim, we achieve this using splitters as well.
  - For reductive AND:
    - Split the signal into individual bits
    - Connect these bits to the inputs of a single AND gate

# Replication and Concatenation

- The binary value 011 (3 in decimal) is the same as 0011 or 000000011.
  - Adding zeros in the most significant bits of a positive or an unsigned number does NOT change the number being represented!
  - Example:
    - If the output of a module is 3-bits and you want to feed it to a 5-bit input of another module, you'd need to use both replication & concatenation!
- In Logisim, this is achieved using **Bit Extender** under Wiring in components.